



Digital Systems VLSI

Nanos Georgios

Topic A2)


The following are the dataflow and behavioral descriptions of the 3-in-8 binary decoder:

Dataflow:

```
library ieee;
use ieee.std_logic_1164.all;
entity decoder3to8 is
    port(
        enc: in std_logic_vector(2 downto 0);
        dec: out std_logic_vector(7 downto 0)
    );
end entity;

architecture dataflow of decoder3to8 is
    begin
        dec(7) <= enc(2) and enc(1) and enc(0);
        dec(6) <= enc(2) and enc(1) and not enc(0);
        dec(5) <= enc(2) and not enc(1) and enc(0);
        dec(4) <= enc(2) and not enc(1) and not enc(0);
        dec(3) <= not enc(2) and enc(1) and enc(0);
        dec(2) <= not enc(2) and enc(1) and not enc(0);
        dec(1) <= not enc(2) and not enc(1) and enc(0);
        dec(0) <= not enc(2) and not enc(1) and not enc(0);
    end dataflow;
```

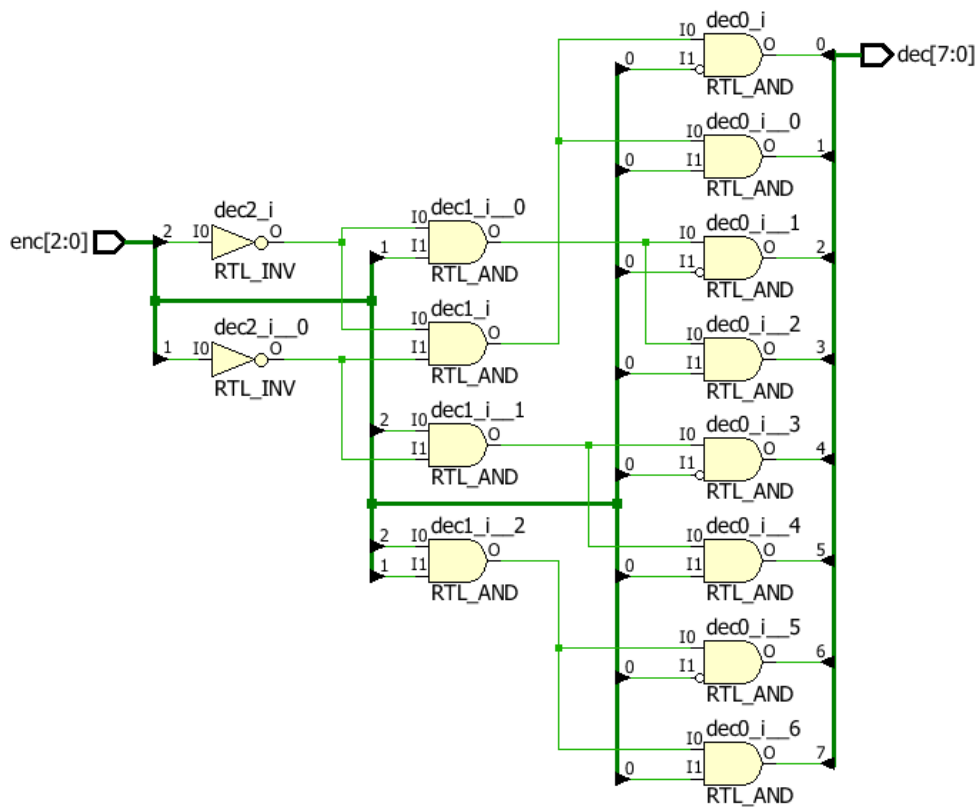The corresponding schematic diagram is as follows:



Behavioural:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity decoder3to8 is
  port(
    enc: in std_logic_vector(2 downto 0);
    dec: out std_logic_vector(7 downto 0)
  );
end entity;

architecture behavioural of decoder3to8 is
begin
  process(enc)
  begin
    case enc is
      when "000" =>
        dec <= "00000001";
      when "001" =>
        dec <= "00000010";
      when "010" =>
        dec <= "00000100";
    end case;
  end process;
end architecture;

```


```

when "011" =>
    dec <= "00001000";
when "100" =>
    dec <= "00010000";
when "101" =>
    dec <= "00100000";
when "110" =>
    dec <= "01000000";
when "111" =>
    dec <= "10000000";
when others =>
    dec <= (others => '-');
end case;
end process;

end architecture;

```

The relevant RTL Schematic:

 

Simulation:

For both different architectures, the same testbench file was used, with the following code:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity decoder3to8_tb is
end entity;

```

architecture bench of decoder3to8_tb is

component decoder3to8 is

```
port (  
    enc: in std_logic_vector(2 downto 0);  
    dec: out std_logic_vector(7 downto 0)  
);  
end component;
```

```
signal enc : std_logic_vector(2 downto 0) := (others => '0');  
signal dec : std_logic_vector(7 downto 0);
```

```
constant CLOCK_PERIOD : time := 10 ns;
```

begin

test : decoder3to8

```
port map (  
    enc => enc,  
    dec => dec  
);
```

stimulus : process

begin

----- Stimulus example -----

for i in 0 to 7 loop -- enc loop

```
    enc <= std_logic_vector(to_unsigned(i, 3));
```

```
    wait for CLOCK_PERIOD;
```

end loop;


```
enc <= (others => '0');
```


```
wait;
```

end process;

end architecture;

 Finally, here is a snapshot of the simulation, in which the input variable is increased in order to constantly change the output value of the decoder:



 

Topic B2)

The following is the description of the requested slider in Behavioural architecture:

```

library ieee;
use ieee.std_logic_1164.all;

entity shift_reg is
    port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          shft : in STD_LOGIC;
          si : in STD_LOGIC;
          en : in STD_LOGIC;
          pl : in STD_LOGIC;
          din : in STD_LOGIC_VECTOR (3 downto 0);
          so : out STD_LOGIC);
end shift_reg;

architecture behavioural of shift_reg is
    signal dff: std_logic_vector(3 downto 0);
begin
    edge: process (clk,rst)
    begin
        if rst='0' then
            dff<=(others=>'0');
            so <= dff(0);
        elsif clk'event and clk='1' then
            if pl='1' then
                dff<=din;
                so<=dff(0);
            elsif en='1' then
                case shft is
                    when '1' =>
                        so<=dff(0);
                        dff<=si&dff(3 downto 1);
                    when '0' =>
                        so<=dff(3);
                        dff<=dff(2 downto 0)&si;
                    when others =>


```

```

        so<='-' ;
        dff<=(others=>'-' );
    end case;
else
    so<='-' ;
    dff<=(others=>'-' );
end if;
end if;
end process;
end behavioural;

```

The corresponding schematic:

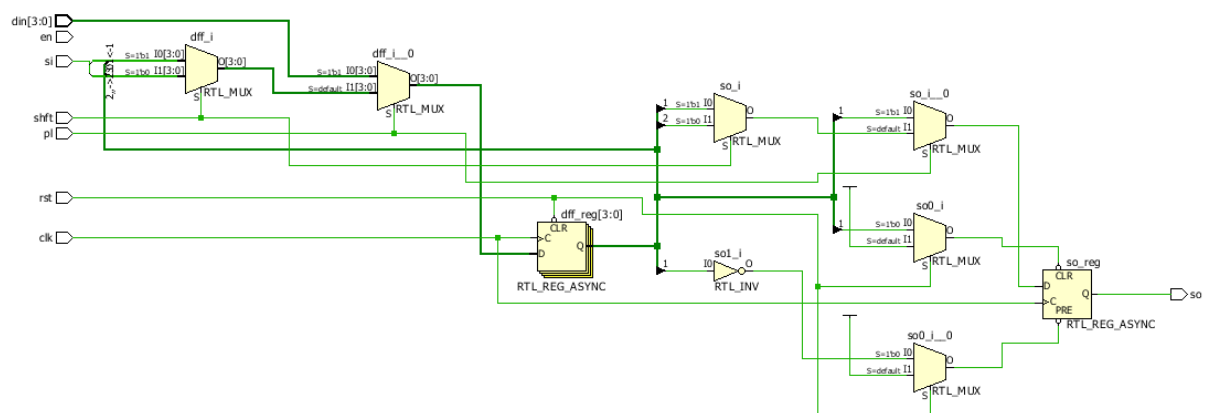

The Testbench file:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity shift_reg_tb is
end entity;

architecture bench of shift_reg_tb is

    component shift_reg is
        port ( clk : in STD_LOGIC;
              rst : in STD_LOGIC;
              shft : in STD_LOGIC;
              si : in STD_LOGIC;
              en : in STD_LOGIC;
              pl : in STD_LOGIC;
              din : in STD_LOGIC_VECTOR (3 downto 0);
              so : out STD_LOGIC);
    end component;

end architecture;
```

```
signal clk : std_logic;
signal rst : std_logic := '0';
signal shft : std_logic := '0';
signal si : std_logic := '0';
signal en : std_logic := '0';
signal pl : std_logic := '0';
signal din : std_logic_vector(3 downto 0) := (others => '0');
signal so : std_logic;
```

```
constant CLOCK_PERIOD : time := 10 ns;
```

```
begin
```

```
test : shift_reg
  port map (clk => clk,
            rst => rst,
            shft => shft,
            si => si,
            en => en,
            pl => pl,
            din => din,
            so => so
```

```
);
```

```
stimulus : process
```

```
begin
```

```
----- Stimulus example -----
```

```
rst <= '0';
din <= (others => '0');
shft <= '0';
si <= '0';
en <= '0';
pl <= '0';
din <= (others => '0');
wait for CLOCK_PERIOD*3;
```

```
rst <= '1';
```

```
pl <= '1';
```

```
for i in 0 to 15 loop
```

```
    din <= std_logic_vector(to_unsigned(i, 4));
```

```
    wait for CLOCK_PERIOD*2;
```

```
end loop;
```

```
din <= (3 => '1',
```

```
        2 => '0',
```

```
        1 => '1',
```

```
        0 => '0');
```

```
wait for CLOCK_PERIOD;
```

```
pl <= '0';
```

```
en <= '1';
```

```

shft <= '1';
si<='1';
for i in 0 to 3 loop
    wait for CLOCK_PERIOD*2;
end loop;

shft <= '0';

for i in 0 to 3 loop
    wait for CLOCK_PERIOD*2;
end loop;

en<='0';

wait for CLOCK_PERIOD;


wait;
end process;


generate_clock : process
begin
    clk <= '0';
    wait for CLOCK_PERIOD/2;
    clk <= '1';
    wait for CLOCK_PERIOD/2;
end process;

end architecture;

```

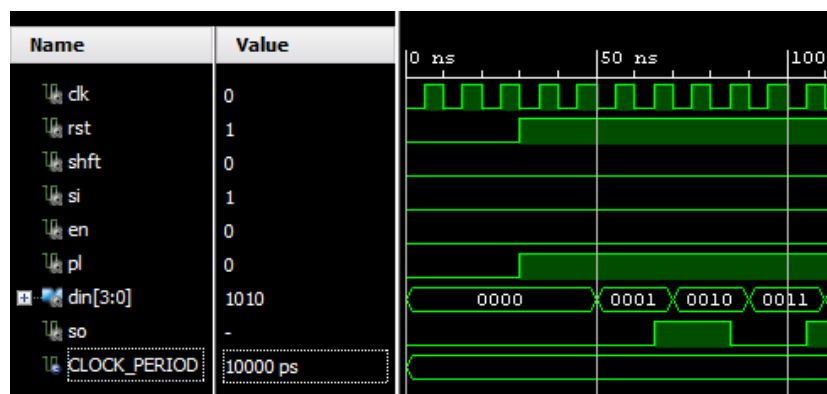And finally, three snapshots of the simulation:



 

Topic B3)

Note: In the following descriptions, the output variable cout takes the value 1 only if the current output of the meter is equal to the maximum value of the meter. In all other cases it is 0.

Up / Down Counter:

Behavioural Architecture:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ex3_count3updown is
  Port ( clk : in std_logic;
        count_en : in std_logic;
        resetn : in std_logic;
        direction : in std_logic;
        cout : out std_logic;
        sum : out std_logic_vector (2 downto 0));
end ex3_count3updown;

architecture behavioural of ex3_count3updown is
  signal count: std_logic_vector(2 downto 0);
begin


  process(clk, resetn)
  begin
    if resetn='0' then
      -- Code for reset
      count <= (others=>'0');
    elsif clk'event and clk='1' then
      if count_en='1' then
```

```

-- Count when count_en=1
case direction is
--0 for down, 1 for up
  when '0'=> count<=count-1;
  when '1'=> count<=count+1;
  when others=> count <= (others=>'0');
end case;
end if;
end if;
end process;
-- Output signals
sum <= count;
cout <= '1' when count=7 and count_en='1' else '0';
end behaviour;

```

The schematic:

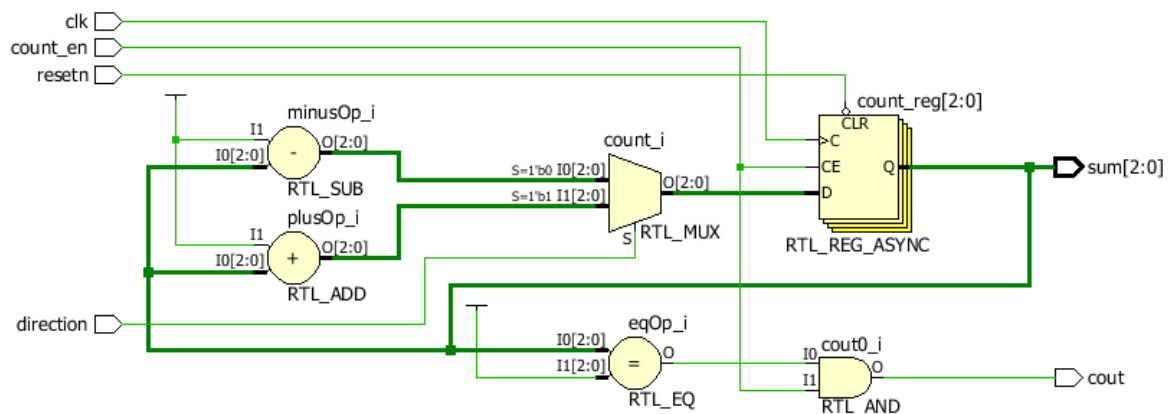

The ***Testbench***:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ex3_count3updown_tb is
end entity;

architecture bench of ex3_count3updown_tb is

  component ex3_count3updown is
    port ( clk : in std_logic;
          count_en : in std_logic;
          resetn : in std_logic;
          direction : in std_logic;

```

```
        cout : out std_logic;
        sum : out std_logic_vector (2 downto 0));
end component;
```

```
signal clk : std_logic := '0';
signal count_en : std_logic := '0';
signal resetn : std_logic := '0';
signal direction : std_logic := '0';
signal cout : std_logic;
signal sum : std_logic_vector (2 downto 0);
```

```
constant CLOCK_PERIOD : time := 10 ns;
```

```
begin
```

```
test : ex3_count3updown
  port map ( clk => clk,
            count_en => count_en,
            resetn => resetn,
            direction => direction,
            cout => cout,
            sum => sum
          );
```

```
stimulus : process
```

```
begin
```

```
--Test reset=0
```

```
count_en <= '1';
```

```
resetn <= '0';
```

```
clk <='1';
```

```
direction <='1';
```

```
for i in 0 to 9 loop
```

```
  clk <= not clk;
```

```
  wait for CLOCK_PERIOD;
```

```
end loop;
```

```
resetn <= '1';
```

```
--Test count up
```

```
for i in 0 to 19 loop
```

```
  clk <= not clk;
```

```
  wait for CLOCK_PERIOD;
```

```
end loop;
```

```
count_en <= '0';
```

```
--Test inactive count
```

```
for i in 0 to 9 loop
```

```
  clk <= not clk;
```

```
  wait for CLOCK_PERIOD;
```

```
end loop;
```

```
--Test count down
```

```
direction <='0';
```

```
count_en <= '1';
```

```

for i in 0 to 23 loop
  clk <= not clk;
  wait for CLOCK_PERIOD;
end loop;

direction <='1';




for i in 0 to 9 loop
  clk <= not clk;
  wait for CLOCK_PERIOD;
end loop;

wait;
end process;

end bench;

```

And the simulation:

   

Meter with parallel measurement input:

Behavioural Architecture:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity ex3_count3up_input is
  Port ( clk : in std_logic;
        count_en : in std_logic;
        resetn : in std_logic;
        paral_input : in std_logic_vector (2 downto 0);
        cout : out std_logic;
        sum : out std_logic_vector (2 downto 0));
end ex3_count3up_input;

architecture behavioural of ex3_count3up_input is
  signal count: std_logic_vector(2 downto 0);
begin

  process(clk, resetn)
  begin
    if resetn='0' then
      -- Code for reset
      count <= (others=>'0');
    elsif clk'event and clk='1' then
      if count_en='1' then
        -- Count up when count_en = 1
        if count/=paral_input then
          -- Increase counter only when not equal to input
          count<=count+1;
        else
          --Else zero
          count<=(others=>'0');
        end if;
      end if;
    end if;
  end process;
  -- Output signals
  sum <= count;
  cout <= '1' when count=paral_input and count_en='1' else '0';

end behavioural;
```

The schematic:

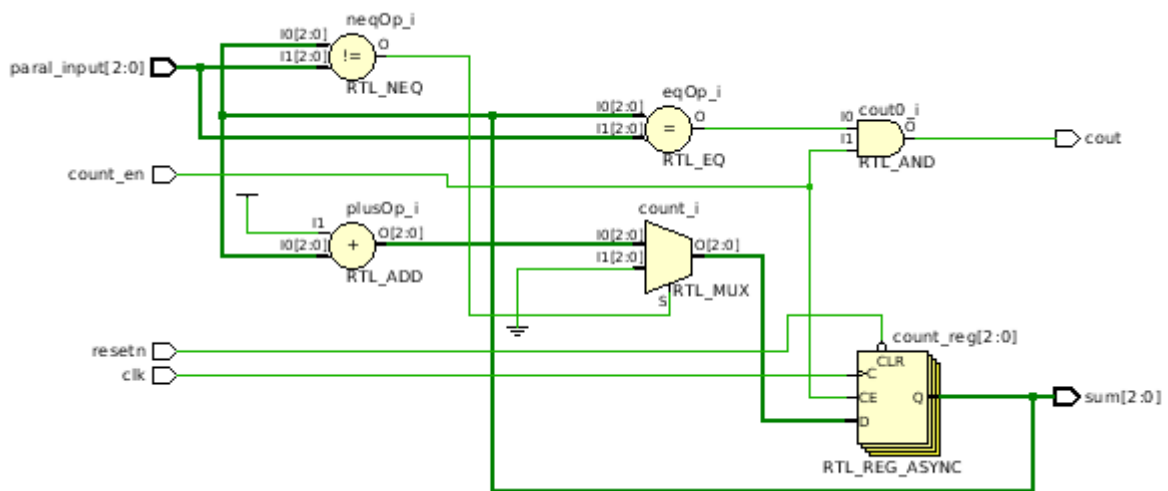

The *testbench*:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ex3_count3up_input_tb is
end entity;

architecture bench of ex3_count3up_input_tb is

    component ex3_count3up_input is
        port ( clk : in std_logic;
              count_en : in std_logic;
              resetn : in std_logic;
              paral_input : in std_logic_vector (2 downto 0);
              cout : out std_logic;
              sum : out std_logic_vector (2 downto 0));
    end component;

    signal clk : std_logic := '0';
    signal count_en : std_logic := '0';
    signal resetn : std_logic := '0';
    signal paral_input : std_logic_vector (2 downto 0) := (others => '0');
    signal cout : std_logic;
    signal sum : std_logic_vector (2 downto 0);

    constant CLOCK_PERIOD : time := 10 ns;

begin

    test : ex3_count3up_input
        port map ( clk => clk,
                  count_en => count_en,
                  resetn => resetn,
                  paral_input => paral_input,

```

```

        cout => cout,
        sum => sum
    );

stimulus : process
begin
    --Test reset=0
    count_en <= '1';
    resetn <= '0';
    clk <='1';
    paral_input <= "101";
    for i in 0 to 9 loop
        clk <= not clk;
        wait for CLOCK_PERIOD;
    end loop;

    resetn <= '1';

    --Test count up with limit '5'
    for i in 0 to 15 loop
        clk <= not clk;
        wait for CLOCK_PERIOD;
    end loop;

    count_en <= '0';
    --Test inactive count
    for i in 0 to 4 loop
        clk <= not clk;
        wait for CLOCK_PERIOD;
    end loop;
    --Test 'change limit to 3'
    paral_input <= "011";

    for i in 0 to 4 loop
        clk <= not clk;
        wait for CLOCK_PERIOD;
    end loop;

    count_en <= '1';

    for i in 0 to 15 loop
        clk <= not clk;
        wait for CLOCK_PERIOD;
    end loop;

    wait;
end process;

end bench;

```

The simulation:

